
Logic and Computer Design Fundamentals

Chapter 2 – Combinational Logic Circuits

Part 4 – HDLs Overview

Ming Cai

cm@zju.edu.cn


College of Computer Science and Technology
Zhejiang University

Overview

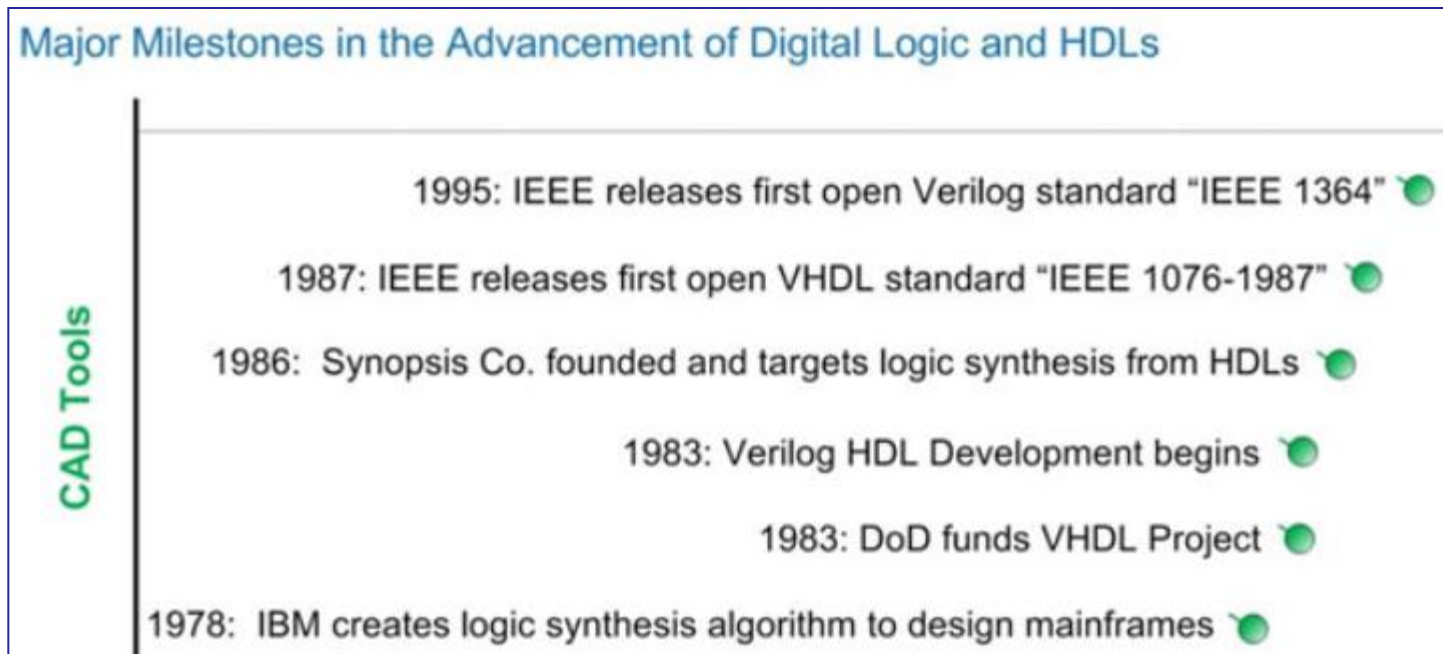
- **Part 4 – HDLs overview**
 - **HDLs Overview**
 - **Logic Synthesis**
 - **HDL Representations—Verilog**

HDLs overview


- A hardware description language (HDL) is a specialized computer language used to **describe** the **structure** and **behavior** of electronic circuits.
- It is feasible to use CAD tools for designing complex digital systems.



Classical Digital Design Flow

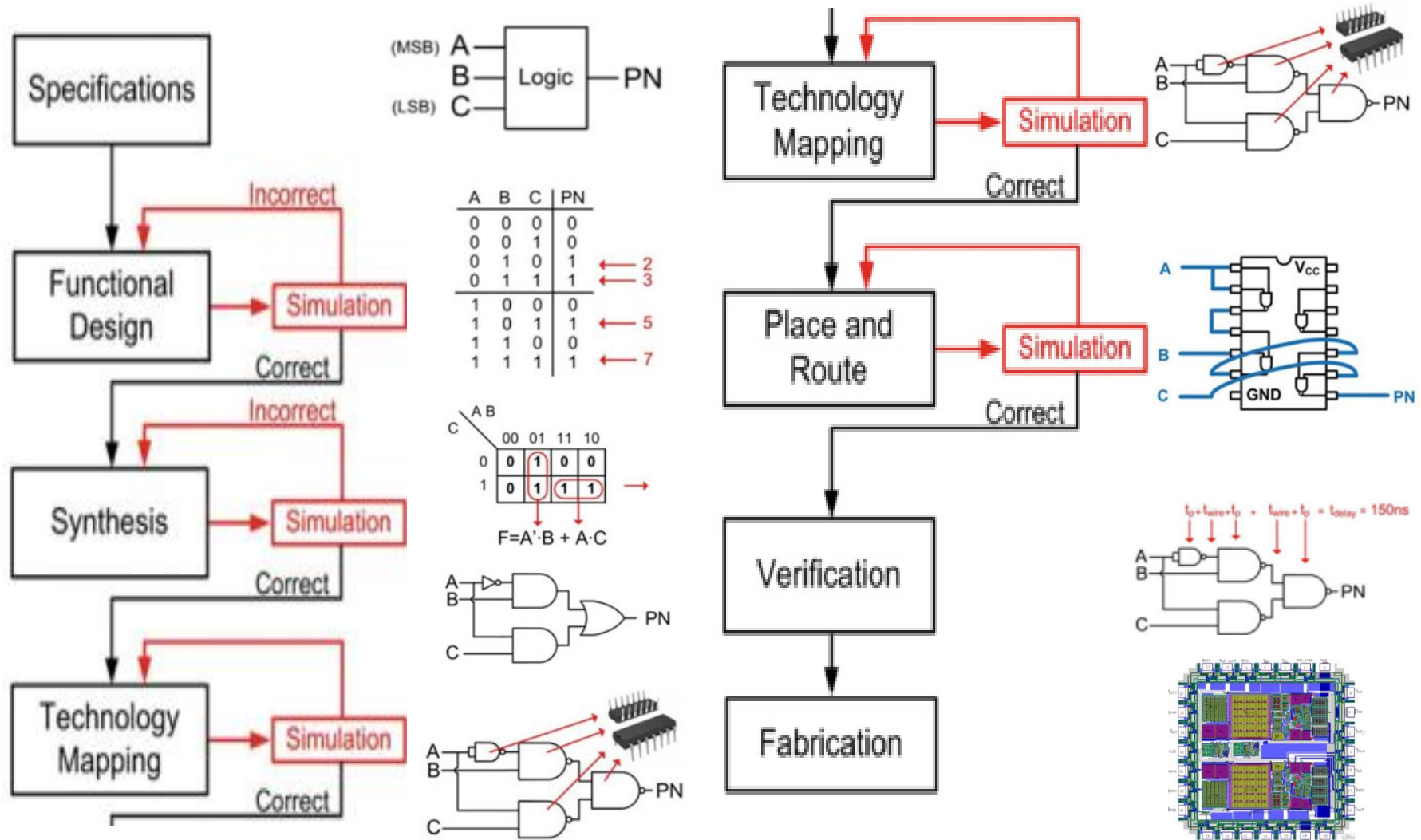


Logic Synthesis

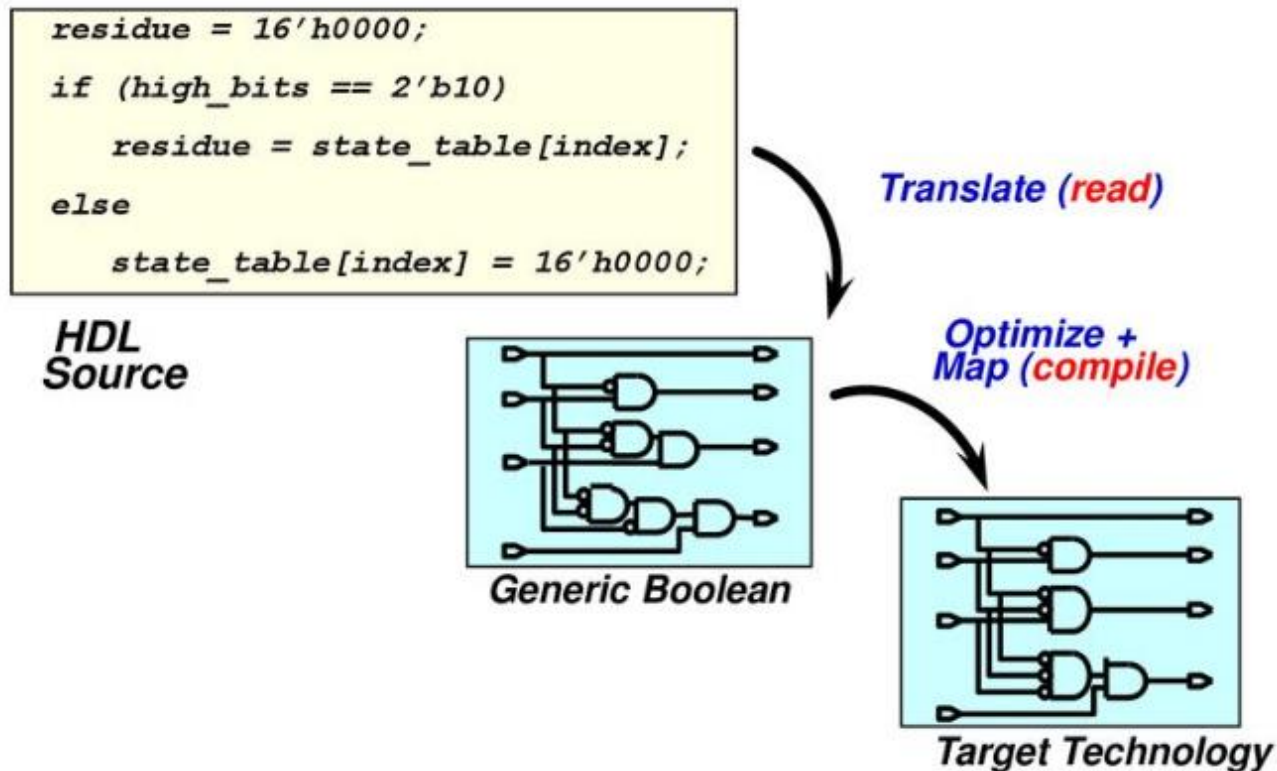

- **Logic synthesis** is a process where a high-level description of the design is converted into an **optimized gate-level representation** given a **standard-cell library** and certain **design constraints** (e.g., area, performance, power).


An Anatomy of a Verilog File

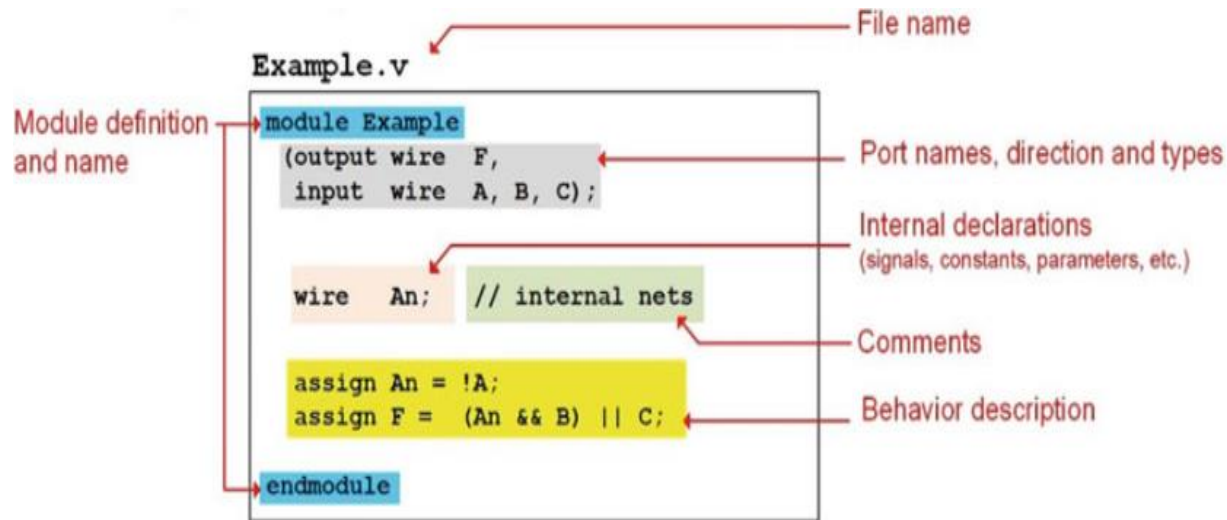

- A Verilog design consists of a **hierarchy of modules**. Modules encapsulate design hierarchy, and communicate with other modules through input, output, and bidirectional ports.
- Use **synthesizable code** to describe the function of circuit that could be built in hardware.
- **Non-synthesizable (delay, loop)** constructs should be used only for test benches.

Describing Hardware with Verilog

 - A two-bit greater-than comparator circuit:
if $(A_1A_0 > B_1B_0)$ $Y=1$; else $Y=0$;




		B_1, B_0			
		00	01	11	10
A_1, A_0	00	0	0	0	0
	01	1	0	0	0
	11	1	1	0	1
	10	1	1	0	0

$$Y = A_1\overline{B}_1 + A_1A_0\overline{B}_0 + A_0\overline{B}_1\overline{B}_0$$

Structural Verilog Description of Two-Bit Greater-Than Circuit

$$Y = A_1\bar{B}_1 + A_1A_0\bar{B}_0 + A_0\bar{B}_1\bar{B}_0$$


```
// Two-bit greater-than circuit: Verilog structural model           // 1
// See Figure 2-27 for logic diagram                               // 2
module comparator_greater_than_structural(A, B, A_greater_than_B); // 3
    input [1:0] A, B;                                              // 4
    output A_greater_than_B;                                       // 5
    wire B0_n, B1_n, and0_out, and1_out, and2_out;
    not
        inv0(B0_n, B[0]), inv1(B1_n, B[1]);
    and
        and0(and0_out, A[1], B1_n),
        and1(and1_out, A[1], A[0], B0_n),
        and2(and2_out, A[0], B1_n, B0_n);
    or
        or0(A_greater_than_B, and0_out, and1_out, and2_out); // 13
endmodule                                                       // 14
                                                                    // 15
```

 

Dataflow Verilog Description of Two-Bit Greater-Than Comparator


$$Y = A_1\bar{B}_1 + A_1A_0\bar{B}_0 + A_0\bar{B}_1\bar{B}_0$$

```
// Two-bit greater-than circuit: Dataflow model // 1
// See Figure 2-27 for logic diagram // 2
module comparator_greater_than_dataflow(A, B, A_greater_than_B); // 3
    input [1:0] A, B; // 4
    output A_greater_than_B;
    wire B1_n, B0_n, and0_out, and1_out, and2_out;
    assign B1_n = ~B[1];
    assign B0_n = ~B[0];
    assign and0_out = A[1] & B1_n;
    assign and1_out = A[1] & A[0] & B0_n;
    assign and2_out = A[0] & B1_n & B0_n; // 11
    assign A_greater_than_B = and0_out | and1_out | and2_out; // 12
endmodule // 13
```

 

Conditional Dataflow Verilog Description of Two-Bit Greater-Than Circuit


```
// Two-bit greater-than circuit: Conditional model           // 1
// See Figure 2-27 for logic diagram                         // 2
module comparator_greater_than_conditional2(A, B, A_greater_than_B); // 3
    input [1:0] A, B;                                         // 4
    output A_greater_than_B;                                  // 5
    assign A_greater_than_B = (A > B)? 1'b1 :                // 6
        1'b0;                                                // 7
endmodule                                                  // 8
```

 

$$Y = A_1 \bar{B}_1 + A_1 A_0 \bar{B}_0 + A_0 \bar{B}_1 \bar{B}_0$$

Behavioral Verilog Description of Two-Bit Greater-Than Circuit

```
// Two-bit greater-than circuit: Behavioral model           // 1
// See Figure 2-27 for logic diagram                       // 2
module comparator_greater_than_behavioral(A, B, A_greater_than_B); // 3
    input [1:0] A, B;                                       // 4
    output A_greater_than_B;                               // 5
    assign A_greater_than_B = A > B;                       // 6
endmodule                                                 // 7
```

 


$$Y = A_1\overline{B}_1 + A_1A_0\overline{B}_0 + A_0\overline{B}_1\overline{B}_0$$

Overview of Verilog Test benches

- A **test bench** supplies the signals and dumps the outputs to simulate a Verilog design.
- Test bench invokes the design under test, generates the simulation **input vectors**, and implements the system tasks to **view the results** of the simulation.
- Test bench uses **non-synthesizable code** to check your synthesizable code.
- Test bench can use all Verilog commands.



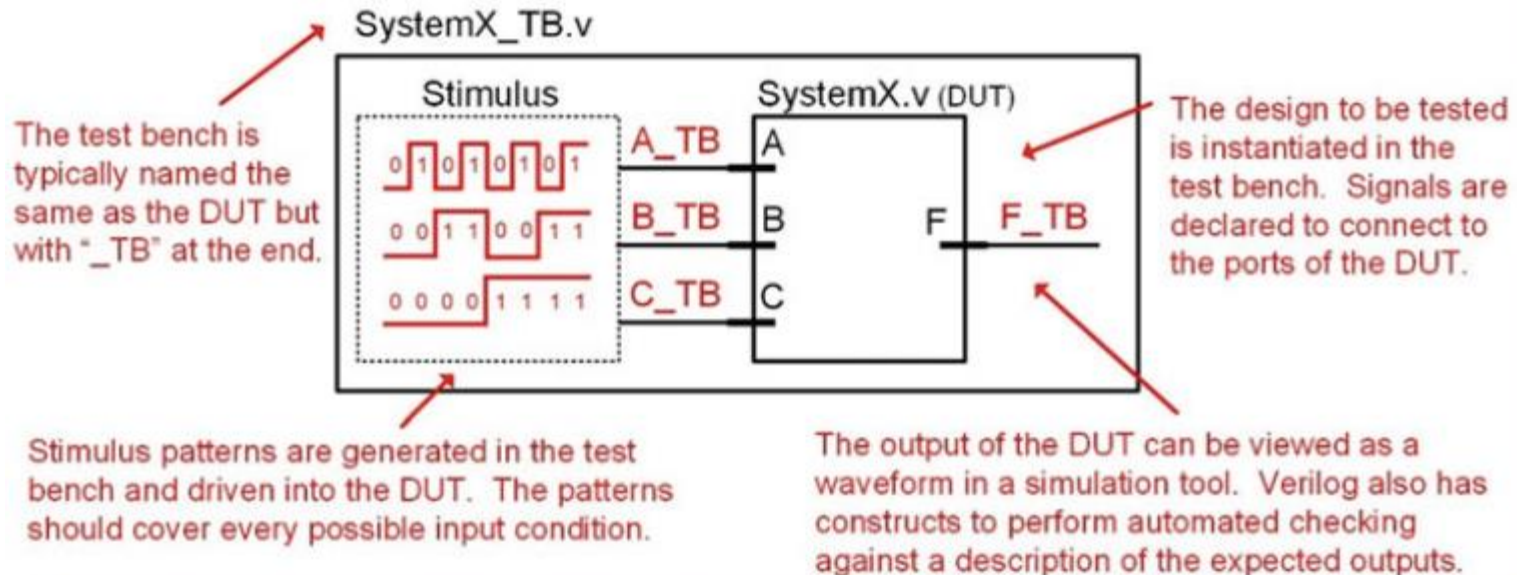
Overview of Verilog Test benches (continued)



```
module SystemX_TB ();  
  
    reg A_TB, B_TB, C_TB;  
    wire F_TB;  
  
    SystemX DUT (F_TB, A_TB, B_TB, C_TB);  
  
    // Stimulus Generation to Drive A_TB, B_TB and C_TB (covered in Ch. 8)  
  
    // Automated Output Checking & Reporting for F_TB (covered in Ch. 8)  
  
endmodule
```

Test bench for the Structural Model of the Two-Bit Greater-Than Comparator

```
// Testbench for Verilog two-bit greater-than comparator // 1
module comparator_testbench_verilog(); // 2
  reg [1:0] A, B; // 3
  wire struct_out; // 4
  comparator_greater_than_structural U1(A, B, struct_out); // 5
  initial // 6
  begin // 7
    A = 2'b10; // 8
    B = 2'b00; // 9
    #10; // 10
    B = 2'b01; // 11
    #10; // 12
    B = 2'b10; // 13
    #10; // 14
    B = 2'b11; // 15
  end // 16
endmodule
```

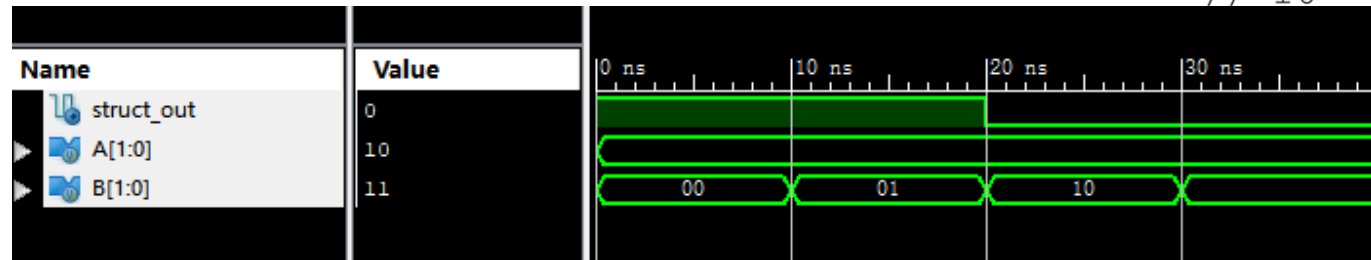  

Assignments

Reading:

- 2.8, 2.10